 


Problem 1:

```

module Prob1 ( input a,
input b,
input c,
input d,
input [1:0] sel,
output out);
assign out = sel[1] ? (sel[0] ? d : c) : (sel[0] ? b : a);
endmodule


```

**Problem 2 :**

```

module Prob2 ( input a,
input b,
input c,
input d,
output[1:0] out);
assign out = d ? 3 : (c ? 2 : (b ? 1 : 0 ));
endmodule

```

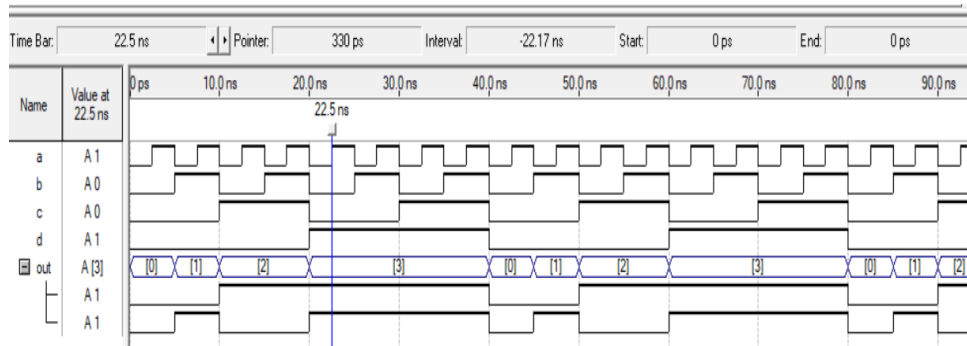


Problem 3:

```
module Prob3 ( input [1:0] a,
output [3:0] out );

assign out = a[1] ? (a[0] ? 8 : 4) : (a[0] ? 2 : 1);

endmodule
```

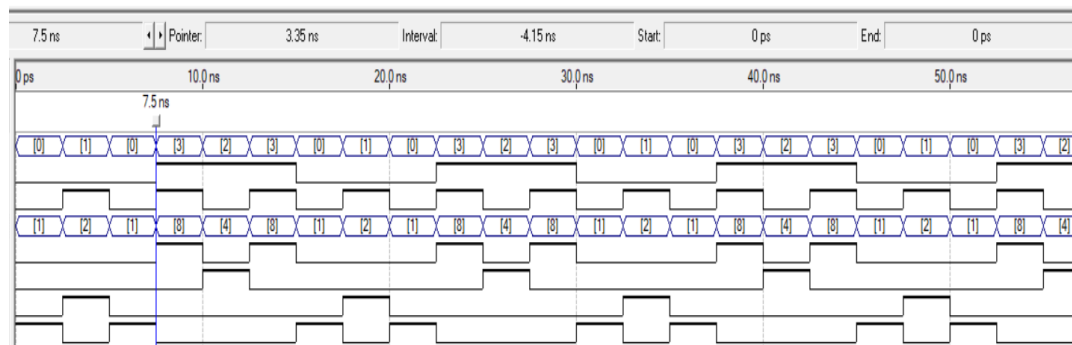

Problem 4:

```
module Prob4(A0,A1,A2,A3,B0,B1,B2,B3,S0,S1,S2,S3,C0,C4,V);

input A0,A1,A2,A3;

input B0,B1,B2,B3;

input C0;

output S0,S1,S2,S3;

output C4,V;

wire A0,A1,A2,A3;

wire B0,B1,B2,B3;
```

```

wire C0;

wire S0,S1,S2,S3;

wire C4,V;

wire C1,C2,C3;

assign X0 = C0^B0;

assign X1 = C0^B1;

assign X2 = C0^B2;

assign X3 = C0^B3;

assign V = C3^C4;

fulladder Y0(C0,X0,A0,S0,C1);

fulladder Y1(C1,X1,A1,S1,C2);

fulladder Y2(C2,X2,A2,S2,C3);

fulladder Y3(C3,X3,A3,S3,C4);

endmodule

module fulladder(a,b,cin,sum,cout);


input a,b,cin;

output sum,cout;

assign {cout,sum} = a+b+cin;


endmodule

```

 

 Problem 5(a):


```
module Prob5a ( din ,x ,y ,a ,b ,c ,d );  
  
output a ;  
  
output b ;  
  
output c ;  
  
output d ;  
  
input din ;  
  
input x ;  
  
input y ;  
  
assign a = din & (~x) & (~y);  
  
assign b = din & (~x) & y;  
  
assign c = din & x & (~y);  
  
assign d = din & x & y;  
  
endmodule
```



 Problem5(b):

```
module Prob5b(  
  
    Clk,  
  
    reset,  
  
    UpOrDown, //high for UP counter and low for Down counter  
  
    Count  
  
);
```

```
input Clk,reset,UpOrDown;
output [3 : 0] Count;
reg [3 : 0] Count = 0;
always @(posedge(Clk) or posedge(reset))
begin
if(reset == 1)
Count <= 0;
else
if(UpOrDown == 1) //Up mode selected
if(Count == 15)
Count <= 0;
else
Count <= Count + 1; //Increment Counter
else //Down mode selected
if(Count == 0)
Count <= 15;
else
Count <= Count - 1; //Decrement counter
end
endmodule
```




Problem 6 Johnson:

```

module Prob6johnson(
    Clock,
    Reset,
    Count_out);
    input Clock;
    output [3:0] Count_out;
    reg [3:0] Count_temp;
    always @(posedge(Clock) or posedge(Reset))
    begin
        if(Reset == 1'b1) begin
            Count_temp = 4'b0000; end
        else if(Clock == 1'b1) begin
            Count_temp = {Count_temp[2:0], ~Count_temp[3]}; end
        end
        assign Count_out = Count_temp;
    endmodule

```

 

Problem 6 Ring Counter:

```
module Prob6ring(q,clk,clr);
```

```
input clk,clr;
```

```
output [3:0] q;
```

```
reg [3:0] a;
```

```
always @(posedge clk)
```

```
if(clr==1)
```

```
a<=4'b1000;
```

```
else
```

```
begin
```

```
a[3]<=a[0];
```

```
a[2]<=a[3];
```


```
a[1]<=a[2];
```

```
a[0]<=a[1];
```

```
end
```

```
assign q = a;
```

```
endmodule
```

 

Problem 7:

```

module Prob7 (Clock, Resetn, a,b, z);
input Clock, Resetn, a,b;
output z;
assign w=a^b;
reg [2:0] y;
parameter [2:0] S0=0, S1=1, S2=2, S3=3, S4=4;
always @(posedge Clock, negedge Resetn)
begin
if (Resetn == 0) y <= S0;
else
begin
case (y)
S0: if (w) y <= S0;
else y <= S1;
S1:
if (w) y <= S0;
else y<=S2;
S2:
if (w) y <= S0;

```



```

else y <= S3;

S3:
if (w) y <= S0;
else y <= S4;

S4:
if (w) y <= S0;
else y <= S4;

endcase


end

end

assign z=(y==S4);

endmodule

```

 

Problem 8:

```

module Prob8(Clock, Resetn, w, z);

input Clock, Resetn, w;

output z;

reg [2:0] y;

parameter [2:0] S0=0, S1=1, S2=2, S3=3;

always @(posedge Clock, negedge Resetn)

begin

```


```

if (Resetn == 0) y <= S0;
else
begin
case (y)
S0: if (w) y <= S3;
    else y <= S2;
S1:
    if (w) y <= S0;
    else y <= S1;
S2:
    if (w) y <= S0;
    else y <= S3;
S3:
    if (w) y <= S1;
    else y <= S1;
endcase
end
end

assign z=(y==S1);

endmodule


```

 

State Diagram:

 7. mealy:

$x = a \text{ XOR } b$, $z = \text{output}$



8.

